
Class B Audio Speaker Driver

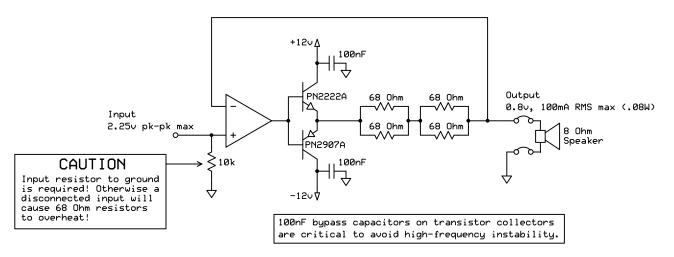
There will be some "cross-over" distortion with this design, but the speakers aren't very good anyway.



The 4x68 Ohm resistors give a total of 1W power dissipation, which is required.

CAUTION

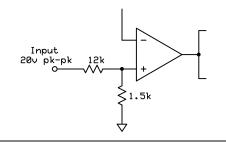Exceeding the pk-pk input voltage limit will cause the output to clip (saturate) and will greatly increase the 68 Ohm resistor power dissipation, so don't do it! Use a voltage divider on the input! (shown below)



Audio Speaker Driver Physics 5/105 F. Rice Rev 1.0 Page 1 of 1